

Ten tips for designing small and efficient AC/DC switching power supplies

CONTENTS

- 1. Input filters
- 2. Inductors and transformers
- 3. Input capacitors
- 4. Input switch
- 5. Silicon carbide (SiC) rectifiers in boost converters
- 6. Control circuits
- 7. Cooling
- 8. Digital control
- 9. Mechanical design
- 10. Component layout

Hiren Shah, Vice President of Engineering gives his top ten tips.

The design of AC/DC power supplies is inevitably evolutionary, rather than revolutionary. It develops largely as a result of gradual improvements in semiconductors and passive component technologies and materials. Invariably, power supply design objectives involve not only meeting basic input and output specifications but also meeting them within a given package size and within tight cost constraints. XP Power has designed several families of AC/DC power supplies in the last couple of years, with output ratings from 40 Watts to 350 Watts. Here are some of the techniques that have worked for us in producing units that both perform to their specifications and meet international standards with respect to EMC performance, safety and input protection. In all of these units, achieving performance objectives within the industry's smallest packages has always been the aim, so many of these tips involve saving space without compromising electrical performance. As far as possible, the ideas are presented in a logical sequence from the input to the output of the power supply.



1. Input filters.

The largest components in input filters are the inductors and capacitors. It pays to keep track of the latest products from all of the main toroid manufacturers as sizes continue to shrink with developments in materials. With respect to Class X (across the line) capacitors, you may be tempted to use ceramic types for their small size. However, these can fail catastrophically in the face of input spikes. Metallized polypropylene types, while larger, cope much better with these spikes as they have an inherent self-healing property. Self-healing removes a fault or short circuit by vaporizing the electrode in the region of the short and restoring the capacitor to useful life. Any loss of capacitance is negligible in normal operation. As with magnetic components, there are gradual reductions in component size over time.

2. Inductors and transformers.

To meet safety requirements with respect to creepage and clearance, a physical safety margin usually has to be left at the edges of bobbins used for winding inductors and transformers. We have found that a triple-insulated, UL-certified, copper wire can remove the need for these gaps; you can then wind right to the edge of the bobbin. This can reduce the overall size of the switching transformer, often the largest component on the board, by as much as 20%.

3. Input capacitors.


Select the working voltage of aluminum electrolytic capacitors carefully to get the best combination of minimum size and good operating life. These capacitors have longer operational life when operated at no more than 80% of their rated voltage. If the capacitors are used at full rated voltage, leakage current produces heating losses that can degrade the components. The rule of thumb is that every 10 degree C increase in temperature halves the life of the capacitor. In practice, the dielectric layer in the capacitors will reform to the voltage at which they are being used, and any voltage surge can result in circuit failure, so the design should take this into account too. Use components with 105 degree C temperature specification for longest operating life. In practice a relatively large capacitor will be needed anyway, not just for ripple reduction but to provide the required DC hold-up time in the event of short-term disruption in the AC input. Typically, a hold up time of 10 – 20 ms is needed. Large electrolytics have high equivalent series resistance (ESR) at higher frequencies, so it's always good practice to include a much smaller capacitor – often a plastic film type, around 0.22 microfarads – in parallel to reduce this.

4. Input switch.

Most designs are based on a DC input to the switch of around 370V (based on $\sqrt{2}$ times the highline AC voltage of 264V). If you use a single MOSFET for switching, the back EMF generated by the stored energy in the input transformer primary when the switch opens will mean that you have to use a 1000VDC rated MOSFET. These are available but they're relatively expensive and have high forward resistance (RDSon) – perhaps as much as

40mOhms – so efficiency is compromised. You'll also need to include a snubber circuit to prevent high voltage spikes damaging the input capacitor and add reset winding in main transformer other components, so component count, cost and board space are all increased. A smarter solution is to use two 500V MOSFET switches (S1 and S2) configured as in Figure 1. The switches operate simultaneously on either side of the transformer secondary and the diodes conduct at approximately 1V above the input voltage, clamping the maximum voltage created by back EMF, protecting the input capacitor and eliminating the need for a snubber circuit. 500V MOSFET switches are around one-sixth of the price of 1000V-rated versions and devices with RDSon as low as 5mOhms are now available from a number of vendors.


Figure 1: Although it minimizes component count, option (A) is more expensive and less efficient than the circuit in (B).

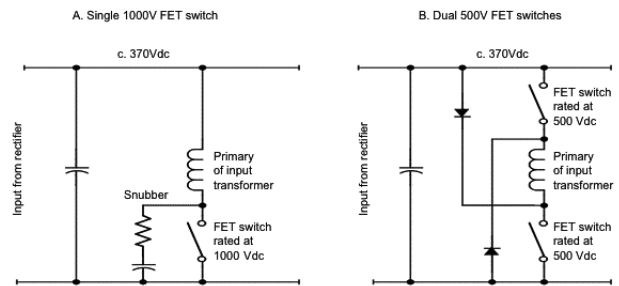

5. Silicon carbide (SiC) rectifiers in boost converters.

These may appear to be expensive but when you calculate the reduction in component count that's possible, the reduced power supply assembly cost, and the savings in board space, you'll probably find that there is no longer an overall cost disadvantage. What's more, you'll find that their use can deliver a 1% improvement in total power supply efficiency. Conventional diodes permit high reverse current and the energy needs to be dissipated in a snubber circuit consisting of 2 diodes, 2 capacitors, a resistor and an inductor, as shown in Figure 2. The negligible reverse current of the SiC diode eliminates these 6 components and reduces losses, leading to improved efficiency. Both Cree and Infineon offer SiC diodes.

Figure 2: The snubber circuit needed with conventional diodes adds cost and complexity

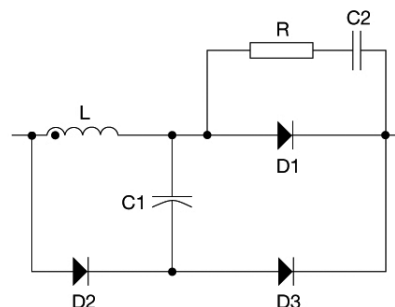

6. Control circuits.

It's now economical to combine through-hole and surface mount techniques in the design of AC/DC switchers. Control functions can be implemented on the underside of the printed circuit board utilizing surface mounted devices.

7. Cooling.

Where possible affix power semiconductors directly to the power supply case or U-channel. You no longer need thermal pastes. Thermal transfer components from companies such as Bergquist allow the tabs of power devices to be soldered directly to a copper pad that is already bonded to an electrically insulating but thermally conductive substrate. This approach is inherently more consistent and reliable than using thermal pastes. Where forced-air cooling is needed, you might consider the use of 3-wire intelligent fans. The fan speed varies with temperature to ensure that the fan only runs as fast as it needs to for given operating conditions. This reduces both noise and power consumption. However, the relatively high prices of these fans, and the ready availability of low cost fan control chips, makes implementing your own control circuit more cost-effective. Fan noise is another consideration. Experiment with the format and spacing of finger guards. We find that placing finger guards a few millimetres away from the panel on which the fan is mounted, rather than flush with it, can reduce fan noise by some 5dB to 6dB. In a system that uses a number of power supplies, this is a very audible reduction.

8. Digital control.

Don't get carried away by all the hype about digital control for AC/DC power supplies, unless your application absolutely needs it. Digital control has been widely implemented in point-of-load converters but it adds considerable cost to AC/DC power supplies. The chips may now be available at 50 cents or so, but when you consider the additional components needed, manufacturing costs and the cost of connectors, implementing digital control will add \$10 to \$15 to the cost of an AC/DC power supply. This may be an acceptable figure for a 1kW power supply, where it is a small proportion of the total cost but for low to medium power units, the additional cost can rarely be justified.

9. Mechanical design.

There is always room for creativity in mechanical design. Consider the range of applications for which the power supply may be used at the outset. For example, it may be possible to design the overall physical dimensions so that the power supply will fit horizontally or vertically into an industry-standard enclosure format. The printed circuit board can be designed to accept plug-in connectors or screw terminals; this adds no cost but greatly improves the application flexibility. And remember the small things, like accessibility of fuses and making cable retention devices reversible, so that the walls of the system enclosure or other protuberances don't obstruct them. Stacking components to save PCB space is another technique that is often overlooked. For example, it may be possible to stack the inductors in a filter

network on top of capacitors, simply fixing them with adhesive. This can also help EMC performance by keeping filter component interconnects very short.

10. Component layout.

To look at some power supplies, you might think that the components were dropped onto the board from a great height and then connected together! Careful component layout, that follows a logical flow from input to output, is good engineering practice. The product looks better, is easier to test and service and it performs better. Remember, every bend in a PCB track adds a little inductance that can create EMI.

XP Power uses all of these techniques in the design of AC/DC power supplies. The company's most recent product, the MFA350 350W AC/DC power supply, shown in Figure 3, uses most of them. The result in this case is an exceptionally compact 3.2" x 6.8" x 1.5" (81mm x 173mm x 38mm) unit, with full control and monitoring features, 89% efficiency and a requirement for only 13CFM of cooling to get full output. No single design innovation has delivered this performance, it the combination of small improvements, such as those outlined above, and that makes a big difference to the end product.

Figure 3: The MFA350, 350 Watt AC/DC switching power supply achieves 11.2W per cubic inch power density



www.xppower.com

North American Sales Offices

Toll Free +1 (800) 253-0490
Central Region +1 (972) 578-1530

Eastern Region +1 (973) 658-8001
Western Region +1 (408) 732-7777

European Sales Offices

Belgium +33 (0)1 45 12 31 15
Denmark +45 43 42 38 33
France +33 (0)1 45 12 31 15
Germany +49 (0)421 63 93 3 0
Italy +39 039 2876027

Netherlands +49 (0)421 63 93 3 0
Norway +47 63 94 60 18
Sweden +46 (0)8 555 367 00
Switzerland +41 (0)56 448 90 80
United Kingdom +44 (0)118 984 5515

Distributors

Australia +61 2 9809 5022 Amtex
Austria +43 (0)2282 3144 Vitcom
Czech Rep. . . +420 235 366 129 Vums Powerprag
Czech Rep. . . +420 377 824 986 Vienna Trading
Finland . . . +358 (0)9 2906 1990 Cool Power
Israel +97 2 9 749 8777 Appletec

Japan +81 48 864 7733 Bellnix
Korea +82 31 421 1404 Bellkor
Portugal +34 93 263 33 54 Venco
Russia +7 (495)234 0636 Prosoft
South Africa . . . +27 11 453 1910 Vepac
Spain +34 93 263 33 54 Venco

Global Catalogue Distributors

AmericasNewark www.newark.com
Europe & Asia Farnell www.farnell.com

North American HQ

XP Power
990 Benecia Avenue
Sunnyvale, CA 94085
Phone : +1 (408) 732-7777
Fax : +1 (408) 732-2002
Email : nasales@xppower.com

European HQ

XP Power
Horseshoe Park
Pangbourne
Berkshire, RG8 7JW
Phone : +44 (0)118 984 5515
Fax : +44 (0)118 984 3423
Email : eusales@xppower.com

Asian HQ

XP Power
401 Commonwealth Drive
Haw Par Technocentre
Singapore 149598
Phone : +65 6411 6900
Fax : +65 6741 8730
Email : apsales@xppower.com



T H E X P E R T S I N P O W E R