

Parallel & Series Operation

CONTENTS

- Parallel Operation
- Series Operation

This is only recommended with power converters specifically designed for parallel connection. A general comment is that it is much lower cost and causes far fewer problems to use a single power converter correctly rated for the application rather than two or more in parallel. However, there are power converters which feature master slave parallel operation. These units are intended for modular expansion schemes and fault tolerant parallel redundant power systems. Where power converters are overload protected by constant current limiting simple parallelling of the outputs can work to an acceptable standard. Output voltages must be set the same (as precisely as possible). In a two unit system the unit with the slightly higher output voltage will reach its current limit and the voltage will drop to equal that of the other unit.



Parallel Operation

This converter will then supply the remaining current demanded by the load. So regulation can never be better than the difference between the output voltage settings of the two converters, and one unit will always be operating in current limit, therefore above its rating. Where current limits are adjustable to below maximum rating simple paralleling is satisfactory if the degradation of regulation can be tolerated. To improve load current sharing, equal series resistors can be used (See Fig. 1).

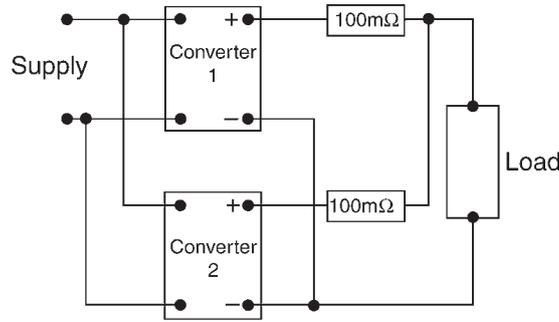


Figure 1. Current sharing resistors used to parallel two converters

For the best results the wiring resistance must also be exactly balanced. Small differences in the output voltage settings of the converter output still creates considerable current unbalance. In the example illustrated, the load is 5V at 2A. Converter output voltage settings are 5V but if they are unequal by 0.1V, the current out of balance from the nominal 1A is 0.5A. This requires that each unit is individually rated at 1.5A. It is clearly not a cost effective method of providing 5V 2A of stabilized power. Also the 100m series resistors degrade the regulation to worse than 2%.

It should be borne in mind that as the output power of the supply rises, the voltage drop and power dissipated rise. The power rating of the resistor should be carefully calculated. At higher currents, the series resistance should be reduced to perhaps 25-30mΩ.

In critical applications where continuous operation is essential, parallel redundant power systems are often specified. The system has to keep running even when a power unit fails. Current sharing is not such an important criterion since each power unit must be rated to supply the total load. But to enable both units to be continuously monitored for faults it is advisable that some measure of current sharing takes place. Both units are then always operating. Isolating series diodes which are continuously rated at the full load current allow either power converter to continue operation unaffected by a fault in the other. Matching the forward resistance of the diodes and balancing the wiring resistance helps with the current sharing. However, these series impedance degrade the regulation. Some power converters, which are specifically designed for use in fault tolerant systems allow remote sense downstream of the paralleling diodes to maintain full regulation at the load. In a parallel redundant scheme one of the power converters could be replaced by a battery followed by a DC-DC converter to provide a no-break power system in the event of main supply failure (See Fig. 2)

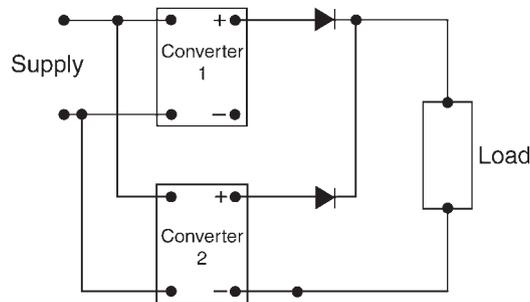


Figure 2. Isolated diodes used for parallel redundant connections of two converters

Series Operation

Most power converters can be operated in series if they have overload limit characteristics, constant current or constant power circuits. With some switching converters series operation is prohibited because one unit upsets the feedback regulation system of the other. With linear and switched mode units using foldback current limiting, lock out at switch ON can occur because of the different ramp up times of two units in series. Care must be taken not to exceed the safe working voltage at the outputs of converters in series. This may be considerably lower than the dielectric strength test voltage which is a short-term test between outputs and ground. The output ripple of converters in series is additive but this of course does not change the value of ripple expressed as a percentage of total output voltage. To protect each output from the reverse voltage applied by the other unit in the event of load short circuits, reverse biased diodes are used. It is common practice to include these protection diodes in laboratory power supplies.

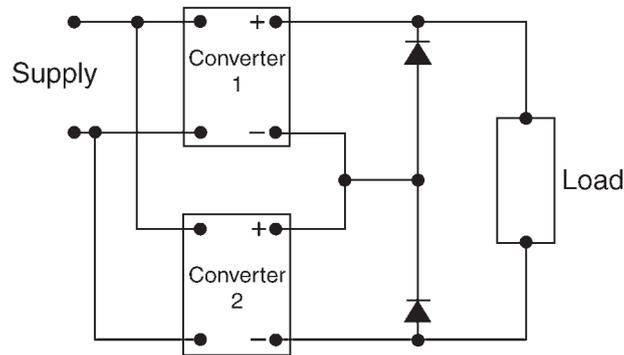


Figure 3. Outputs connected in series showing reverse voltage protection diodes

www.xppower.com

North American HQ

XP Power
990 Benecia Avenue, Sunnyvale, CA 94085
Phone : +1 (408) 732-7777
Fax : +1 (408) 732-2002
Email : nasales@xppower.com

North American Sales Offices

Toll Free.....+1 (800) 253-0490
Central Region.....+1 (972) 578-1530
Eastern Region+1 (973) 658-8001
Western Region.....+1 (408) 732-7777

European HQ

XP Power
Horseshoe Park, Pangbourne,
Berkshire, RG8 7JW, UK
Phone : +44 (0)118 984 5515
Fax : +44 (0)118 984 3423
Email : eusales@xppower.com

German HQ

XP Power
Auf der Höhe 2, D-28357
Bremen, Germany
Phone : +49 (0)421 63 93 3 0
Fax : +49 (0)421 63 93 3 10
Email : desales@xppower.com

European Sales Offices

Austria+41 (0)56 448 90 80
Belgium+33 (0)1 45 12 31 15
Denmark+45 43 42 38 33
Finland.....+46 (0)8 555 367 01
France+33 (0)1 45 12 31 15
Germany.....+49 (0)421 63 93 3 0
Italy+39 039 2876027
Netherlands+49 (0)421 63 93 3 0
Norway.....+47 63 94 60 18
Sweden +46 (0)8 555 367 00
Switzerland..... +41 (0)56 448 90 80
United Kingdom.....+44 (0)118 984 5515

Global Catalog Distributors

AmericasNewark newark.com
Europe & Asia.....Farnell farnell.com
China.....Premier Electronics premierelectronics.com.cn

Asian HQ

XP Power
401 Commonwealth Drive, Haw Par Technocentre, Lobby B,
#02-02, Singapore 149598
Phone : +65 6411 6900
Fax : +65 6741 8730
Email : apsales@xppower.com
Web : www.xppowerchina.com / www.xppower.com

Asian Sales Offices

Shanghai +86 21 51388389
Singapore..... +65 6411 6902

Distributors

Australia+61 2 9809 5022 Amtex
Balkans+386 1 583 7930 Elbacomp
Czech Rep.+420 235 366 129 Vums Powerprag
Czech Rep.+420 539 050 630 Koala Elektronik
Estonia+372 6228866 Elgerta
Greece+30 210 240 1961 ADEM Electronics
Israel+972 9 7498777 Appletec
Japan+81 48 864 7733 Bellnix
Korea+82 31 422 8882 Hanpower
Latvia+371 67501005 Caro
Lithuania.....+370 5 2652683 Elgerta
Poland.....+48 22 8627500 Gamma
Portugal.....+34 93 263 33 54 Venco
Russia+7 (495)234 0636 Prosoft
Russia+7 (812)325 5115 Gamma
South Africa.....+27 11 453 1910 Vepac
Spain.....+34 93 263 33 54 Venco
Taiwan+886 3 3559642 Fullerton Power
Turkey+90 212 465 7199 EMPA



T H E X P E R T S I N P O W E R